

RUTGERS UNIVERSITY

PHYSICS 2 LAB

Resistance

Authors:

Brittney, Kishan, Abhi

Teacher:

James

SIGNATURES

July 27, 2013

Part 1a - resistance of a light-bulb

Procedure and Goal

We have a light-bulb. We send varying amounts of current through the light-bulb. We then measure the voltage across the light-bulb for each current. Our goal is to see if the the resistance of the light-bulb is dependent on the current supplied to it.

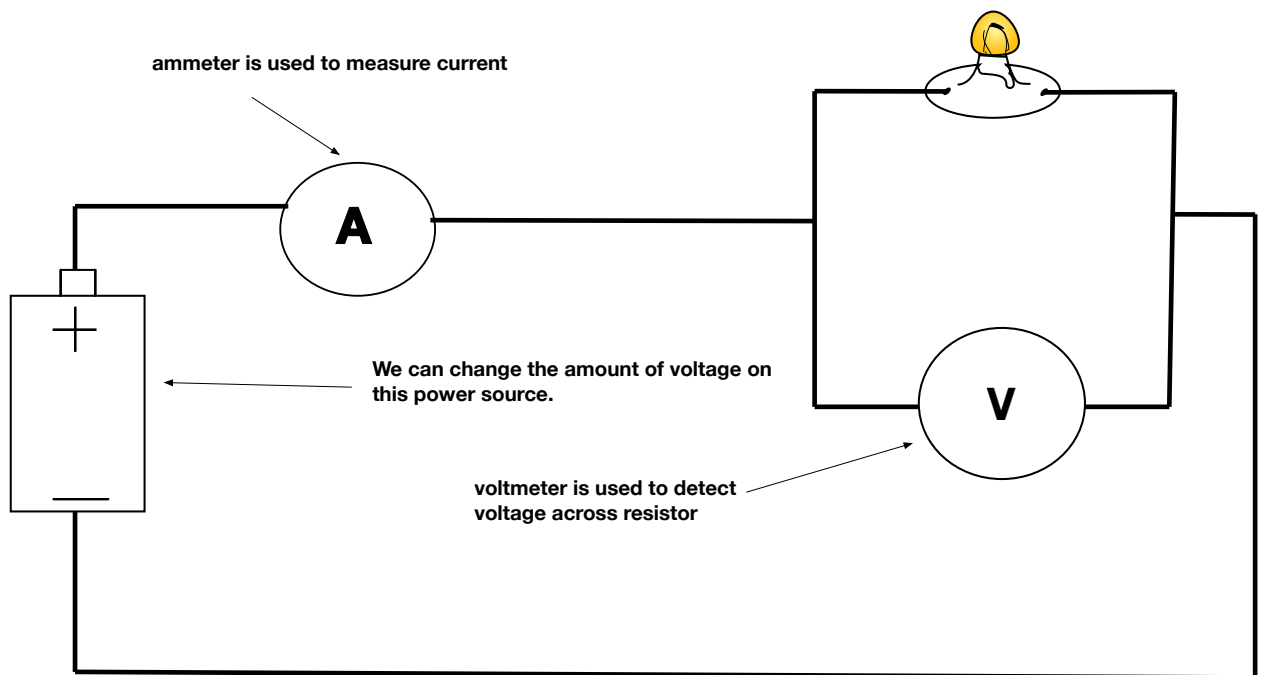


Figure 1: the circuit of our experiment

Prediction

We can follow these steps to show more current \Rightarrow more resistance

1. More current \Rightarrow brighter light-bulb
2. brighter light-bulb \Rightarrow more heat
3. more heat \Rightarrow more resistance

4. therefore we can conclude more current \Rightarrow more resistance

we can say more current \Rightarrow more resistance but can not guess the exact relationship between the current supplied and resistance

Results and Analysis

Here are the results we achieved.

current supplied	voltage across light-bulb	resistance of light-bulb
.03	.39	13
.04	.67	16.75
.05	.98	19.6
.06	1.5	25
.07	1.93	27.5
.08	2.5	31

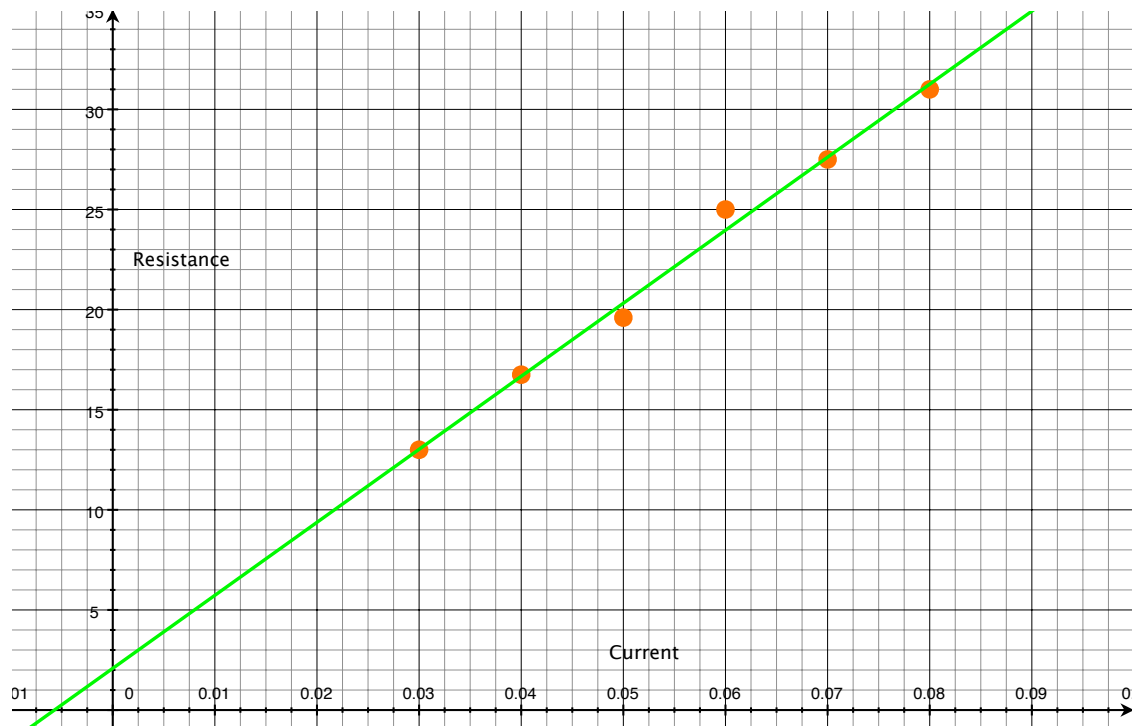


Figure 2: plotting the resistance as a function of current

Our prediction was correct. We found out that the resistance of the light-bulb is directly proportional to the current supplied. The best fit curve we got was $R = 364.71I + 2.08$.

Part 1b - ohmic resistance

Procedure and goal

In this part we repeat part 1a except we replace the light-bulb with a resistance box. We set the box's resistance to 50.

Prediction

Since the box has a fixed relationship, there should be no relation between current and resistance. Resistance should stay fixed at 50.

Results and Analysis

current supplied	voltage across light-bulb	resistance of light-bulb
.02	1	50
.03	1.7	56.6
.05	2.5	50
.06	2.9	56.6
.07	3.4	55.71
.08	4.3	53

In the second part of this experiment our prediction was correct. The resistance recorded stayed at around 50, so the box is an ohmic resistor. The