

## Part 1a - resistance of a light-bulb

### Procedure and Goal

We have a light-bulb. We send varying amounts of current through the light-bulb. We then measure the voltage across the light-bulb for each current. Our goal is to see if the the resistance of the light-bulb is dependent on the current supplied to it.

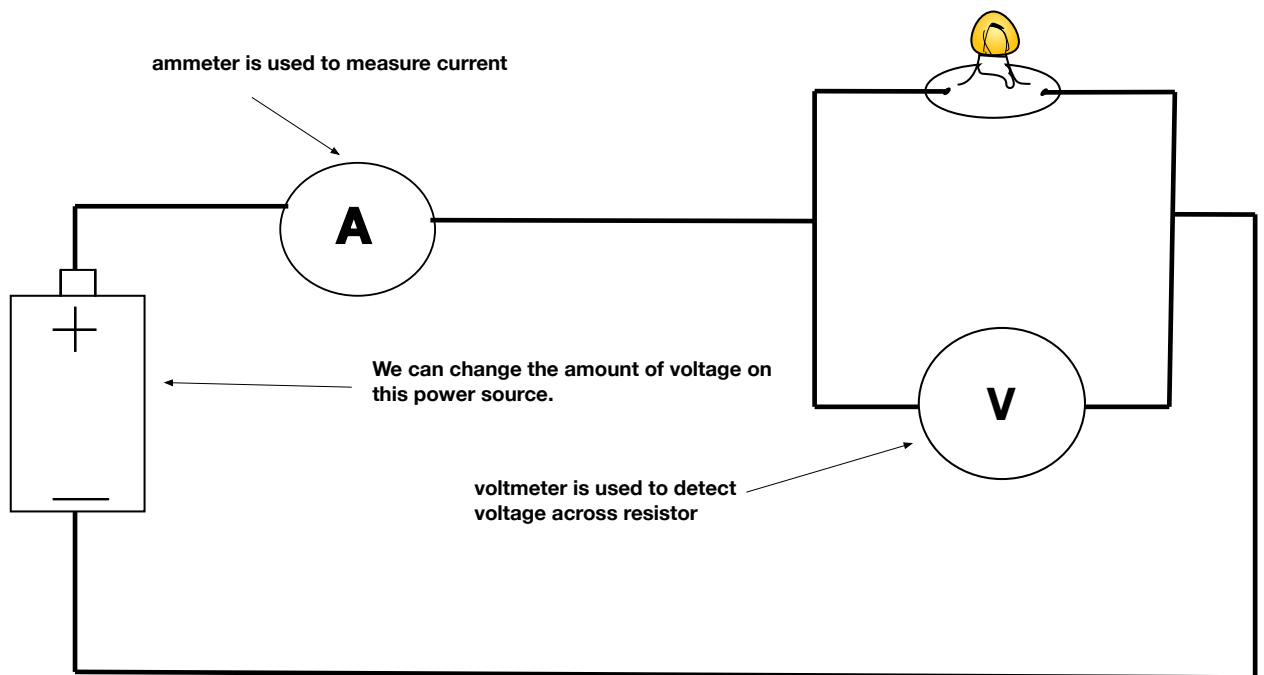


Figure 1: the circuit of our experiment

### Prediction

We can follow these steps to show more current  $\Rightarrow$  more resistance

1. More current  $\Rightarrow$  brighter light-bulb
2. brighter light-bulb  $\Rightarrow$  more heat
3. more heat  $\Rightarrow$  more resistance

4. therefore we can conclude more current  $\Rightarrow$  more resistance

we can say more current  $\Rightarrow$  more resistance but can not guess the exact relationship between the current supplied and resistance

## Results and Analysis

Here are the results we achieved.

current supplied	voltage across light-bulb	resistance of light-bulb
.03	.39	13
.04	.67	16.75
.05	.98	19.6
.06	1.5	25
.07	1.93	27.5
.08	2.5	31

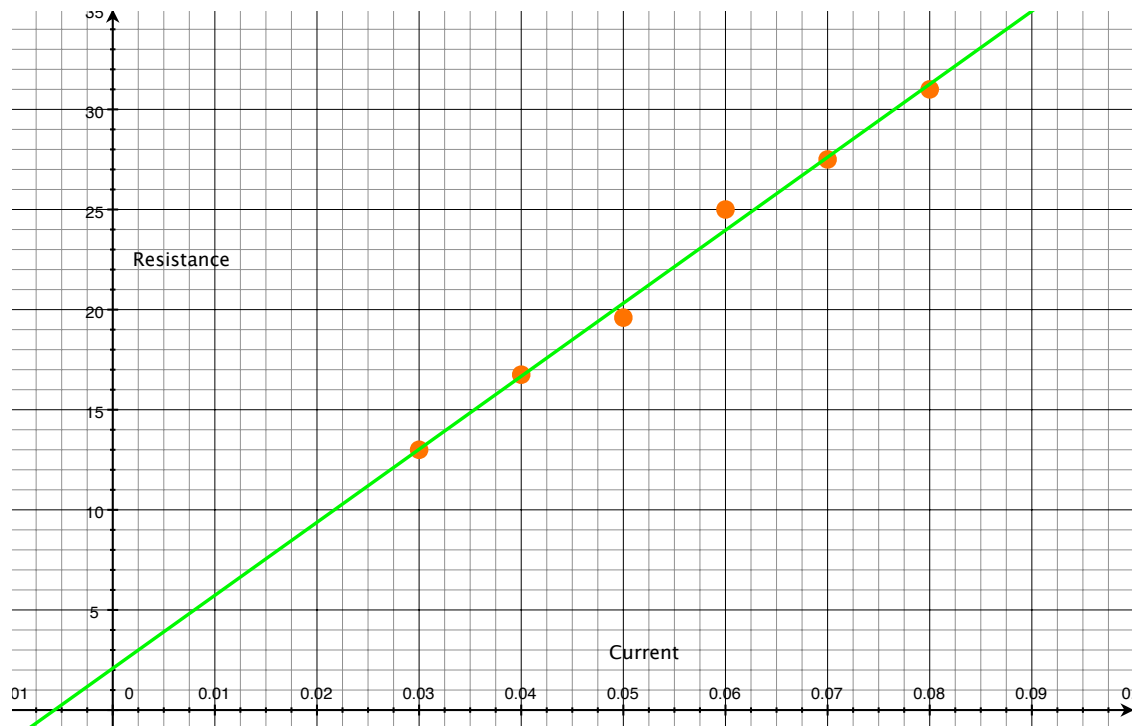


Figure 2: plotting the resistance as a function of current

Our prediction was correct. We found out that the resistance of the light-bulb is directly proportional to the current supplied. The best fit curve we got was  $R = 364.71I + 2.08$ .

## Part 1b - ohmic resistance

### Procedure and goal

In this part we repeat part 1a except we replace the light-bulb with a resistance box. We set the box's resistance to 50.

### Prediction

Since the box has a fixed relationship, there should be no relation between current and resistance. Resistance should stay fixed at 50.

### Results and Analysis

current supplied	voltage across light-bulb	resistance of light-bulb
.02	1	50
.03	1.7	56.6
.05	2.5	50
.06	2.9	56.6
.07	3.4	55.71
.08	4.3	53

In the second part of this experiment our prediction was correct. The resistance recorded stayed at around 50, so the box is an ohmic resistor.